

# Processor Logic Design

# Lesson-11:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Processor organization	<ul style="list-style-type: none"><li>• To understand the bus organization, memory organization, etc.</li><li>• To know the importance of scratchpad memory and accumulator register.</li><li>• Compare different processor organization</li></ul>	Class Lecture Question and answer	Test, exams, quiz, etc

# Introduction

## ❑ Terminologies


- Processor unit
  - Processes digital data
- Control Unit
  - Specifies the operation to be performed by processor
- CPU
  - Combination of processor and control unit
- ALU
  - A combinational circuit which is able to perform arithmetic and logical operations.

# Processor Organization

## □ Bus Organization

Perform

$$R1 \leftarrow R2 + R3$$

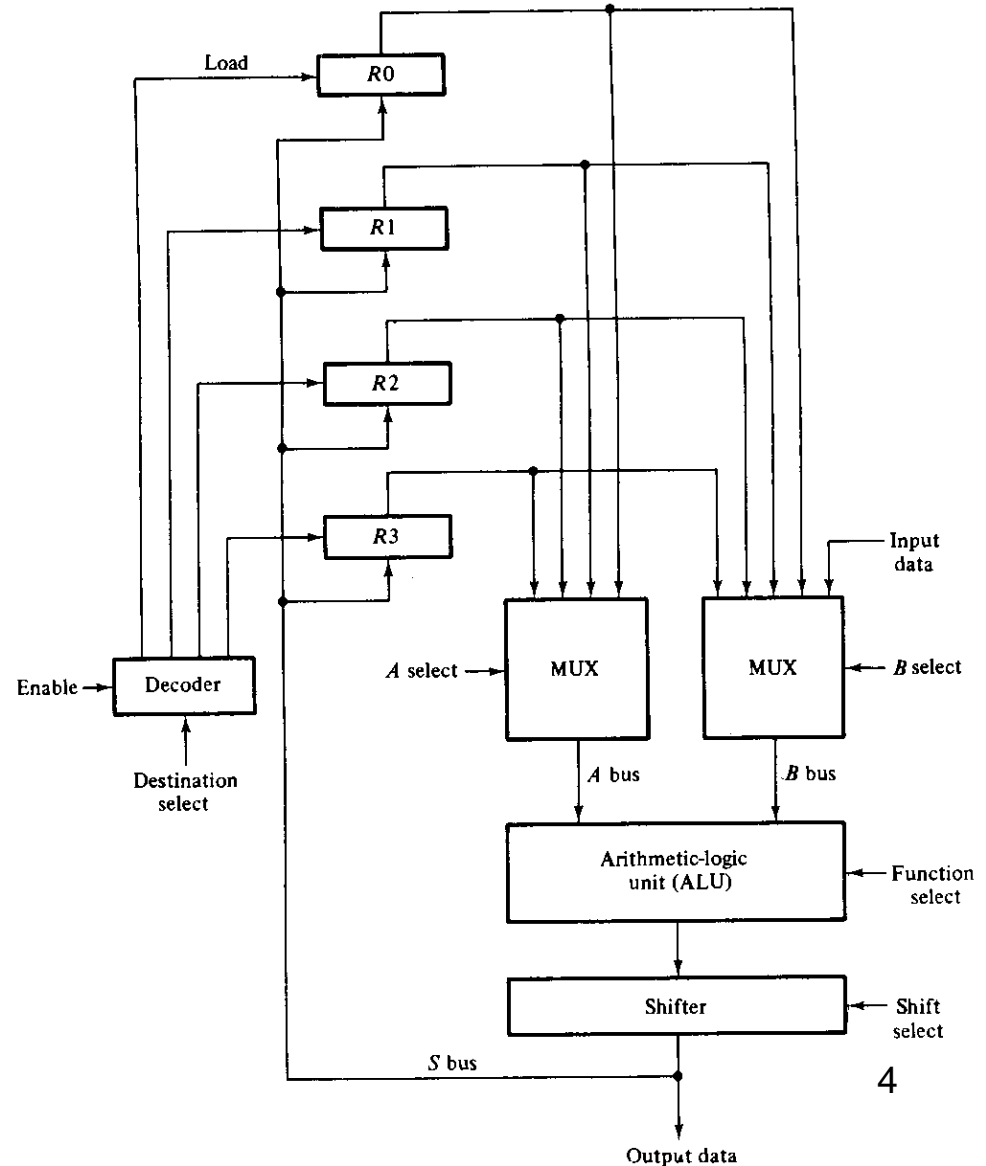

# Processor Organization

## ❑ Scratchpad memory


- Alternative to many registers a single memory unit can be used
- Such memory unit is called scratchpad memory.
- It is different from the main memory.
- Figure shows a processor with scratchpad memory

# Processor Organization

❑ Scratchpad memory

Perform

$R1 \leftarrow R2 + R3$

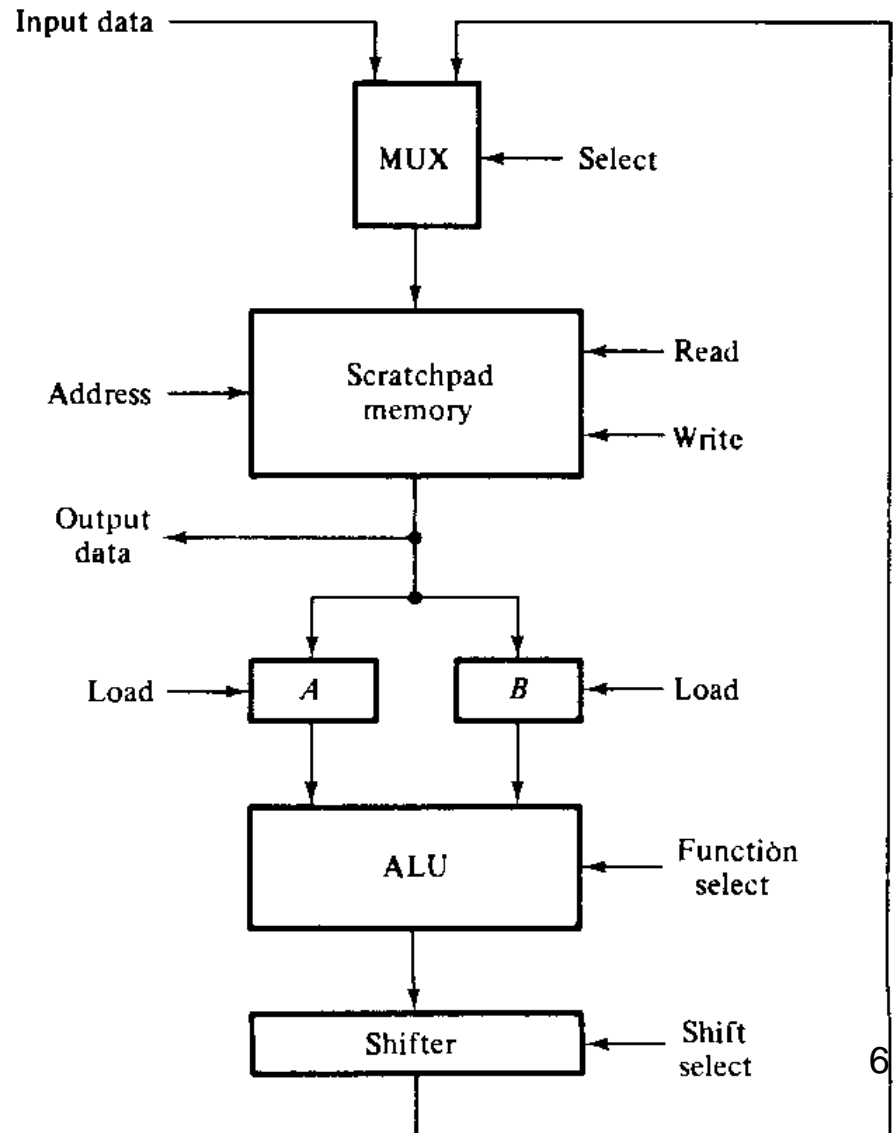


# Processor Organization

## □ Two-port Scratchpad memory

Perform

$$R1 \leftarrow R2 + R3$$

 


# Processor Organization

## ❑ Accumulator Register

- Different from other memory registers
- Used to perform serial addition

Perform

$$R1 \leftarrow R2 + R3$$

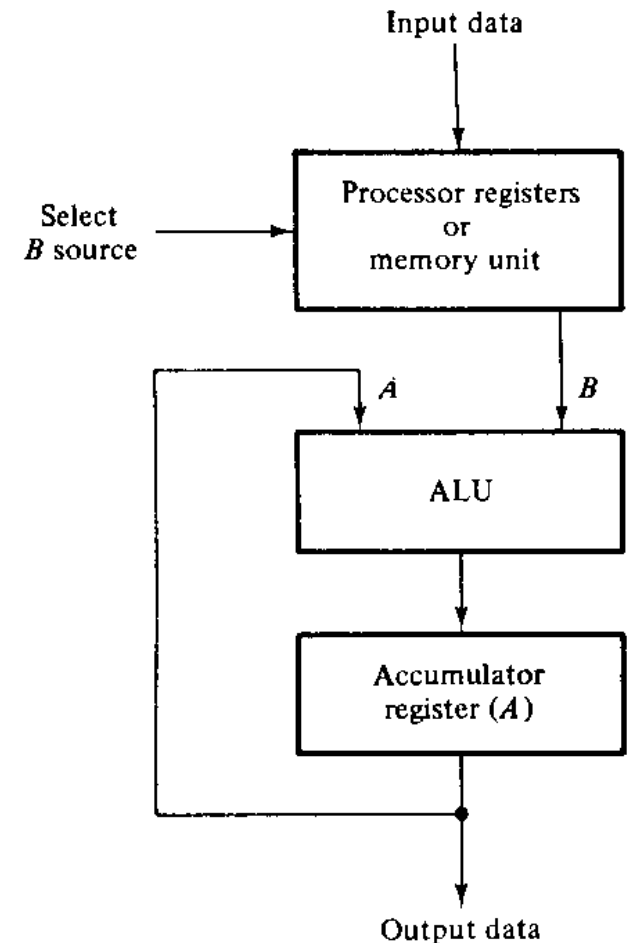




# Processor Organization

- Generic Datapath

Perform

$$R1 \leftarrow R2 + R3$$

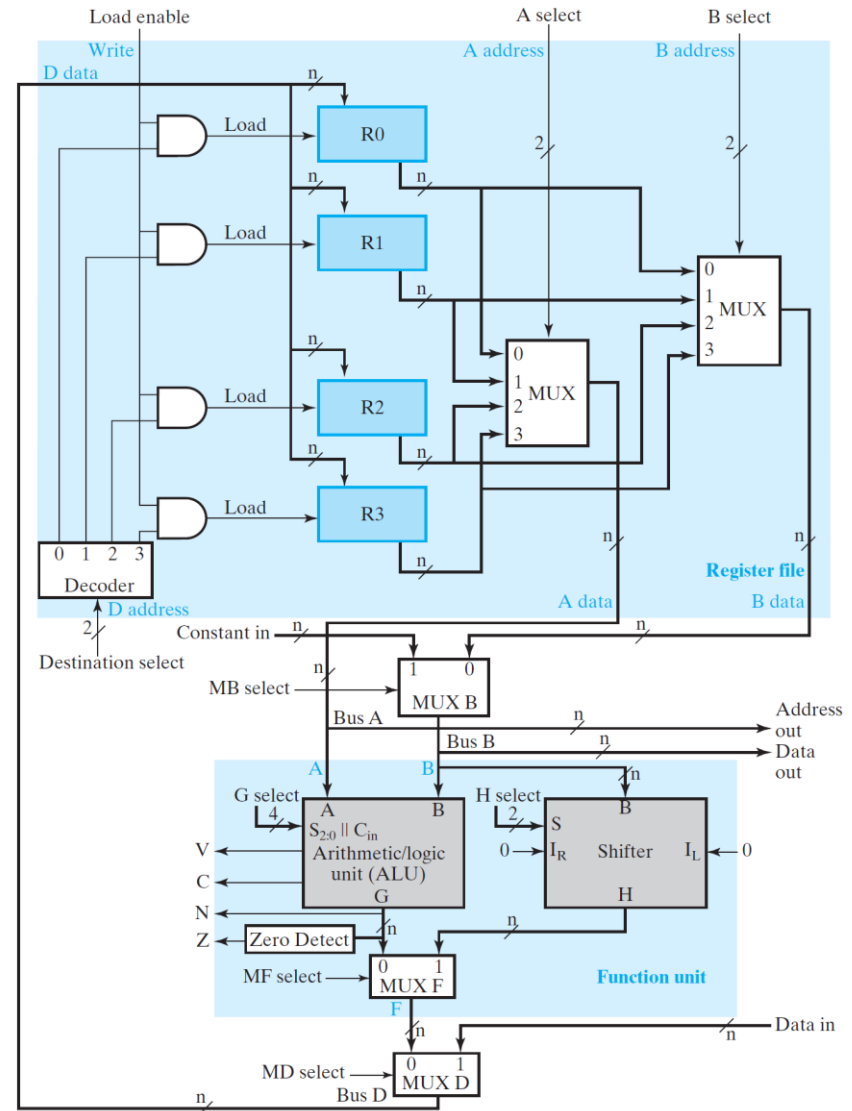


# Lesson-12:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Arithmetic unit	<ul style="list-style-type: none"><li>• To understand the design principles of arithmetic unit</li><li>• To design arithmetic unit with a given set of arithmetic operations.</li></ul>	Class Lecture PBL (Solving some problems in class)	Test, exams, quiz, etc

# Arithmetic Logic Unit
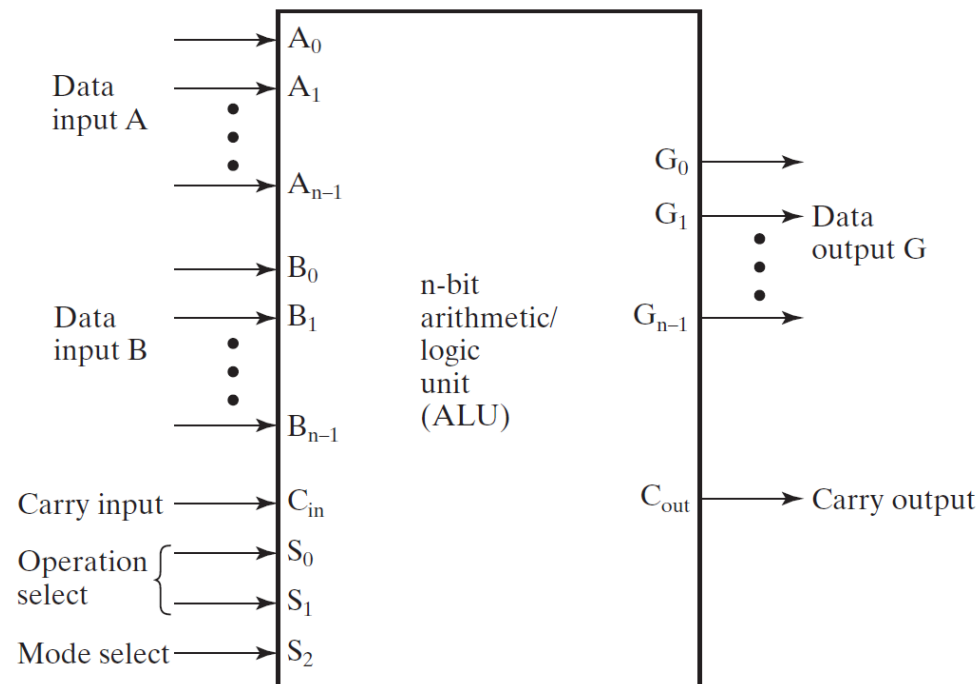
## □ The ALU


- Multi-operational Combinational Circuit.
- Fig. Shows a n-bit ALU
- Design Steps
  - **Design of Arithmetic Unit.**
  - **Design of Logic Unit**
  - **Combine the above two.**



# Arithmetic Logic Unit
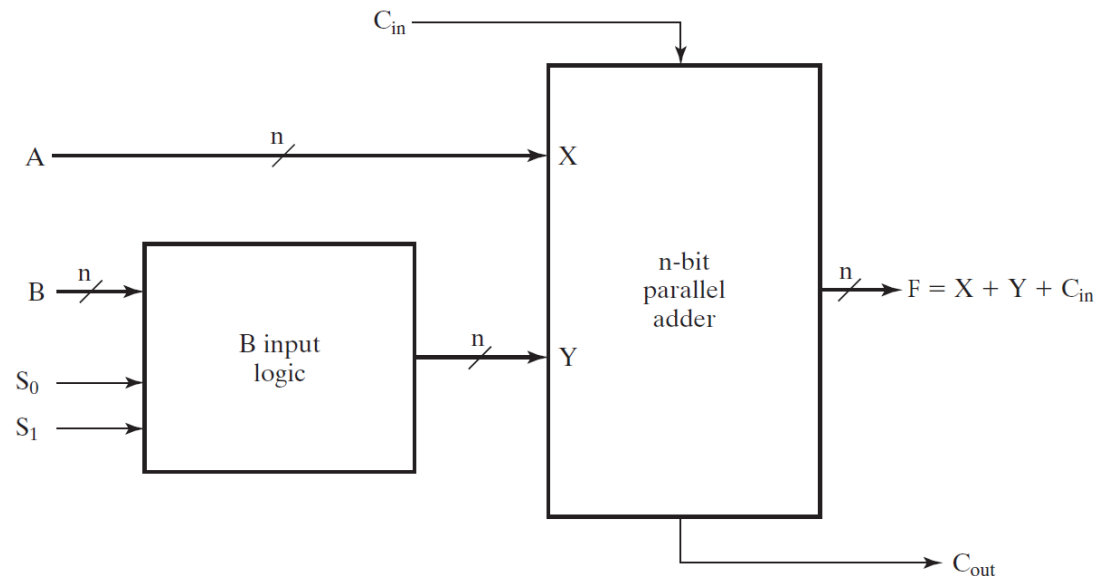
## □ Design of Arithmetic Unit

- Basic component is a parallel-adder.
- Fig. shows a n-bit arithmetic circuit
- Basic operations to be performed by the full-adder
  - **Addition**
  - **Subtraction**
  - **Increment**
  - **Decrement**
  - **Transfer**











# Arithmetic Logic Unit

## □ Parallel-adder

- Operations performed by changing only one variable of PA

Select		Input	$F = (A + Y + C_{in})$	
$S_1$	$S_0$	$Y$	$C_{in} = 0$	$C_{in} = 1$
0	0	all 0s	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	$B$	$G = A + B$ (add)	$G = A + B + 1$
1	0	$\bar{B}$	$G = A + \bar{B}$	$G = A + \bar{B} + 1$ (subtract)
1	1	all 1s	$G = A - 1$ (decrement)	$G = A$ (transfer)

        


# Arithmetic Logic Unit

## □ Design of Arithmetic Unit


- To combine all these operations we need 2 selection variables along with carry.
- **Note that the operations can be performed only by changing the B input and the carry.**
- **The selection circuit**

Inputs			Output
$S_1$	$S_0$	$B_i$	$Y_i$
0	0	0	0 $Y_i = 0$
0	0	1	0
0	1	0	0 $Y_i = B_i$
0	1	1	1
1	0	0	1 $Y_i = \overline{B_i}$
1	0	1	0
1	1	0	1 $Y_i = 1$
1	1	1	1

(a) Truth table

 

 (b) Map simplification:  
 $Y_i = B_i S_0 + \overline{B_i} S_1$



$s_1$	$s_0$	$Y_i$
0	0	0
0	1	$B_i$
1	0	$B_i'$
1	1	1


# Arithmetic Logic Unit

## □ Design of Arithmetic Unit

– The logic diagram

$$X_i = A_i$$
 
$$Y_i = B_i s_0 + B'_i s_1 \quad i = 1, 2, \dots, n$$



Function select			Y equals	Output equals	Function
$s_1$	$s_0$	$C_{in}$			
0	0	0	0	$F = A$	Transfer $A$
0	0	1	0	$F = A + 1$	Increment $A$
0	1	0	$B$	$F = A + B$	Add $B$ to $A$
0	1	1	$B$	$F = A + B + 1$	Add $B$ to $A$ plus 1
1	0	0	$\bar{B}$	$F = A + \bar{B}$	Add 1's complement of $B$ to $A$
1	0	1	$\bar{B}$	$F = A + \bar{B} + 1$	Add 2's complement of $B$ to $A$
1	1	0	All 1's	$F = A - 1$	Decrement $A$
1	1	1	All 1's	$F = A$	Transfer $A$

# Arithmetic Logic Unit

## □ Design other arithmetic circuit


- **Example:** Design an arithmetic circuit with
  - When  $s=0$  perform  $A+B$
  - When  $s=1$  perform  $A-B$
- **Solution**
  - $A+B$  requires
    - $C_{in}=0$ ,  $X_i=A_i$  and  $Y_i=B_i$
  - $A-B$  requires
    - $C_{in}=1$ ,  $X_i=A_i$  and  $Y_i=B_i'$



# Arithmetic Logic Unit

## □ Design other arithmetic circuit

S=0 : Perform A+B  
S=1 : Perform A-B

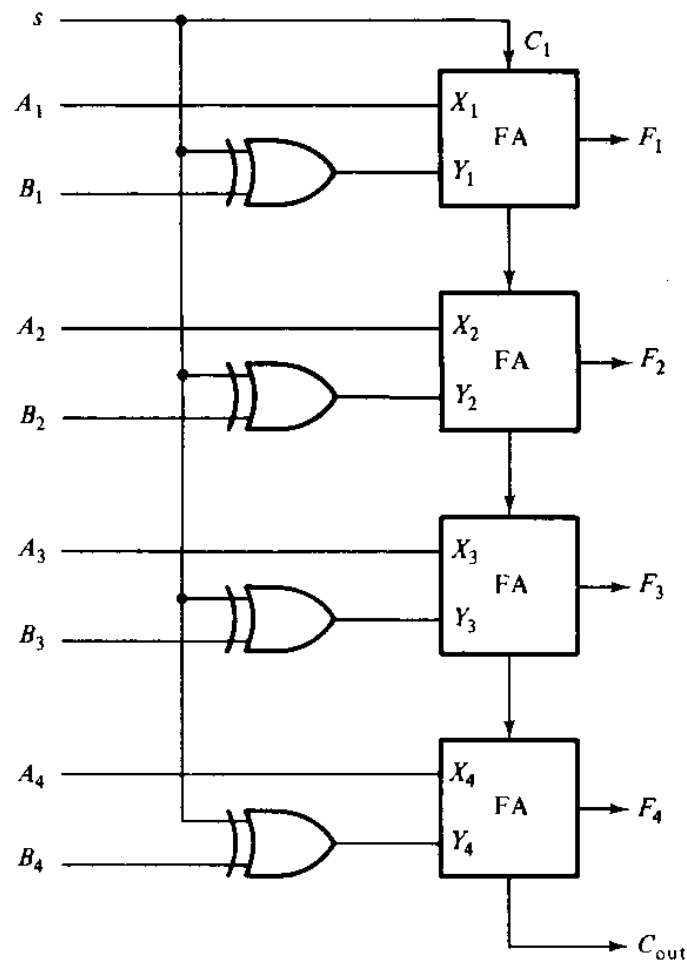


# Lesson-13:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Logical Unit and ALU	<ul style="list-style-type: none"><li>• To design of logical unit</li><li>• To design ALU by combining arithmetic and logic unit.</li></ul>	Class Lecture PBL (Solving some problems in class)	Test, exams, quiz, etc

# Arithmetic Logic Unit

## □ Design of Logic Unit

 


(a) Logic diagram

$s_1$	$s_0$	Output	Operation
0	0	$F_i = A_i + B_i$	OR
0	1	$F_i = A_i \oplus B_i$	XOR
1	0	$F_i = A_i B_i$	AND
1	1	$F_i = A_i'$	NOT

(b) Function table

# Arithmetic Logic Unit

## Combining Arithmetic and Logic Unit

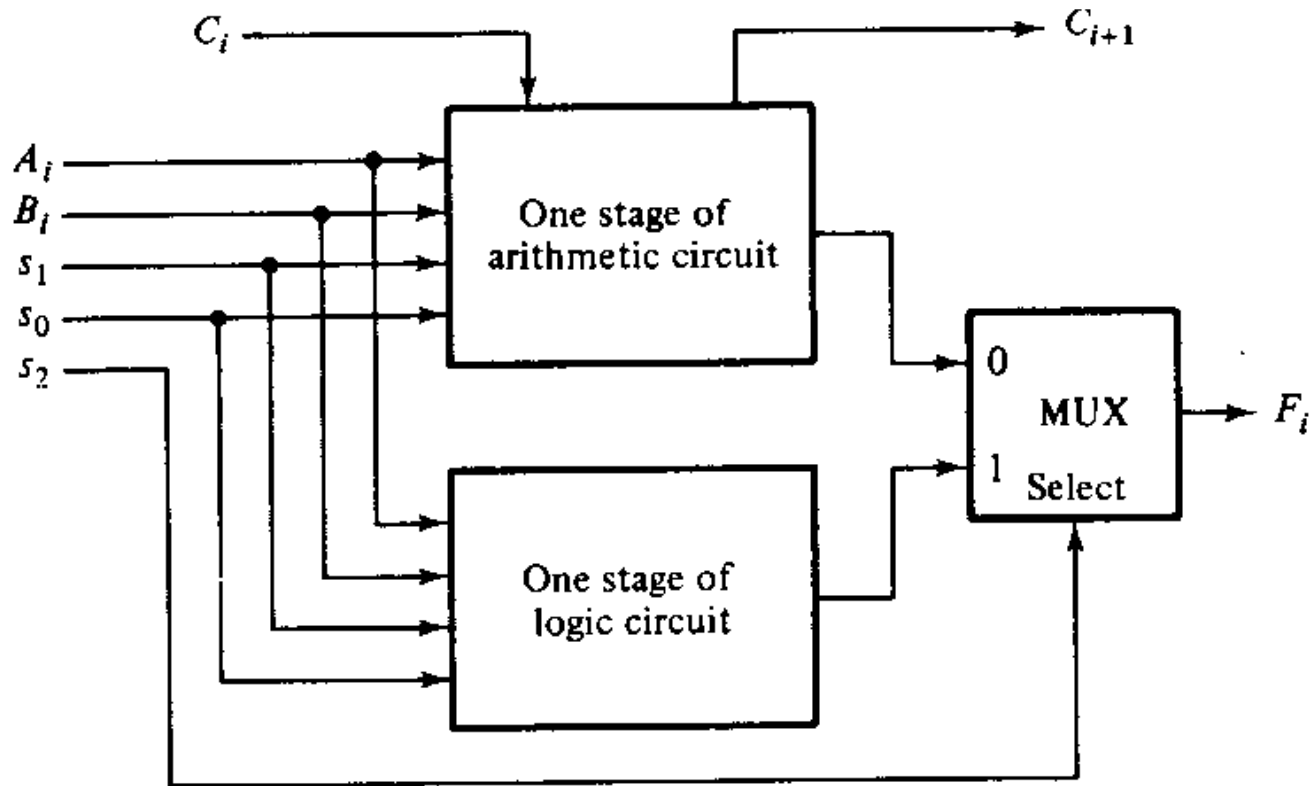

# Arithmetic Logic Unit

## □ How to Design More Efficient ALU

- Note
  - Full-adder with  $C_{in}=0$  performs XOR
  - Table lists the possible operations

$s_2$	$s_1$	$s_0$	$X_i$	$Y_i$	$C_i$	$F_i = X_i \oplus Y_i$	Operation	Required operation
1	0	0	$A_i$	0	0	$F_i = A_i$	Transfer $A$	OR
1	0	1	$A_i$	$B_i$	0	$F_i = A_i \oplus B_i$	XOR	XOR
1	1	0	$A_i$	$B_i'$	0	$F_i = A_i \odot B_i$	Equivalence	AND
1	1	1	$A_i$	1	0	$F_i = A_i'$	NOT	NOT

- Therefore, more efficient ALU design may be possible

# Arithmetic Logic Unit

- More Efficient ALU

- With  $s_2s_1s_0=100$

- $Y_i=0$ , hence we need to change  $X_i$  from  $A_i$  to  $A_i+B_i$

- With  $s_2s_1s_0=110$

- Lets make a similarity with previous case
    - Change  $X_i$  from  $A_i$  to  $A_i+K_i$

$s_2$	$s_1$	$s_0$	$X_i$	$Y_i$	$C_i$	$F_i = X_i \oplus Y_i$	Operation	Required operation
1	0	0	$A_i$	0	0	$F_i = A_i$	Transfer $A$	OR
1	0	1	$A_i$	$B_i$	0	$F_i = A_i \oplus B_i$	XOR	XOR
1	1	0	$A_i$	$B_i'$	0	$F_i = A_i \odot B_i$	Equivalence	AND
1	1	1	$A_i$	1	0	$F_i = A_i'$	NOT	NOT

$$F_i = X_i \oplus Y_i = (A_i + K_i) \oplus B_i' = A_i B_i + K_i B_i + A_i' K_i' B_i'$$

- Consider  $K_i = B_i'$

$$F_i = A_i B_i + B_i' B_i + A_i B_i B_i' = A_i B_i$$

# Arithmetic Logic Unit

- More Efficient ALU
  - Finally the inputs of the full adders are

$$X_i = A_i + s_2 s'_1 s'_0 B_i + s_2 s_1 s'_0 B'_i$$

$$Y_i = s_0 B_i + s_1 B'_i$$

$$Z_i = s'_2 C_i$$

- If  $s_2=0$


$$X_i = A_i$$

$$Y_i = s_0 B_i + s_1 B'_i$$

$$Z_i = C_i$$

# Arithmetic Logic Unit

## More Efficient ALU

 




# Lesson-14:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Status register and shifter in ALU	<ul style="list-style-type: none"><li>• To understand the design principle of Complete ALU and its components</li><li>• To know the importance and use of status register in ALU.</li><li>• To design shift register by using combinational circuit.</li></ul>	Class Lecture PBL (Solving some problems in class)	Test, exams, quiz, etc

# Arithmetic Logic Unit

## □ Status Register

 

# Arithmetic Logic Unit

□ Status bits after subtraction of two unsigned numbers (**A-B**)

Relation	Condition of status bits	Boolean function
$A > B$	$C = 1$ and $Z = 0$	$CZ'$
$A \geq B$	$C = 1$	$C$
$A < B$	$C = 0$	$C'$
$A \leq B$	$C = 0$ or $Z = 1$	$C' + Z$
$A = B$	$Z = 1$	$Z$
$A \neq B$	$Z = 0$	$Z'$


# Design of Shifter

## □ The Shift Unit

- Connected after ALU.
  - **Bidirectional Shift register with parallel load can be used.**
    - **But it requires 3 clock-pulses**
  - **A combination circuit that can perform shift operation is a good choice**
    - **Requires only one clock-puls.**

# Design of Shifter

## □ Combinational Shift Unit

 

# Design of Shifter


## □ Function table of the shifter

$H_1$	$H_0$	Operation	Function
0	0	$S \leftarrow F$	Transfer $F$ to $S$ (no shift)
0	1	$S \leftarrow \text{shr } F$	Shift-right $F$ into $S$
1	0	$S \leftarrow \text{shl } F$	Shift-left $F$ into $S$
1	1	$S \leftarrow 0$	Transfer 0's into $S$

# Design of Shifter
 
## □ Barrel shifter

- Often the data must be shifted more than one bit position in a single clock cycle.
- A *barrel shifter* is designed to do this as shown in Fig.




# Lesson-15:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Processor Unit	<ul style="list-style-type: none"><li>• To construct a processor unit by using the designed ALU</li><li>• To understand the control word of processor and how they can use to perform various microoperations</li></ul>	Class Lecture Question and answer	Test, exams, quiz, etc




# Processor Unit

## Block Diagram

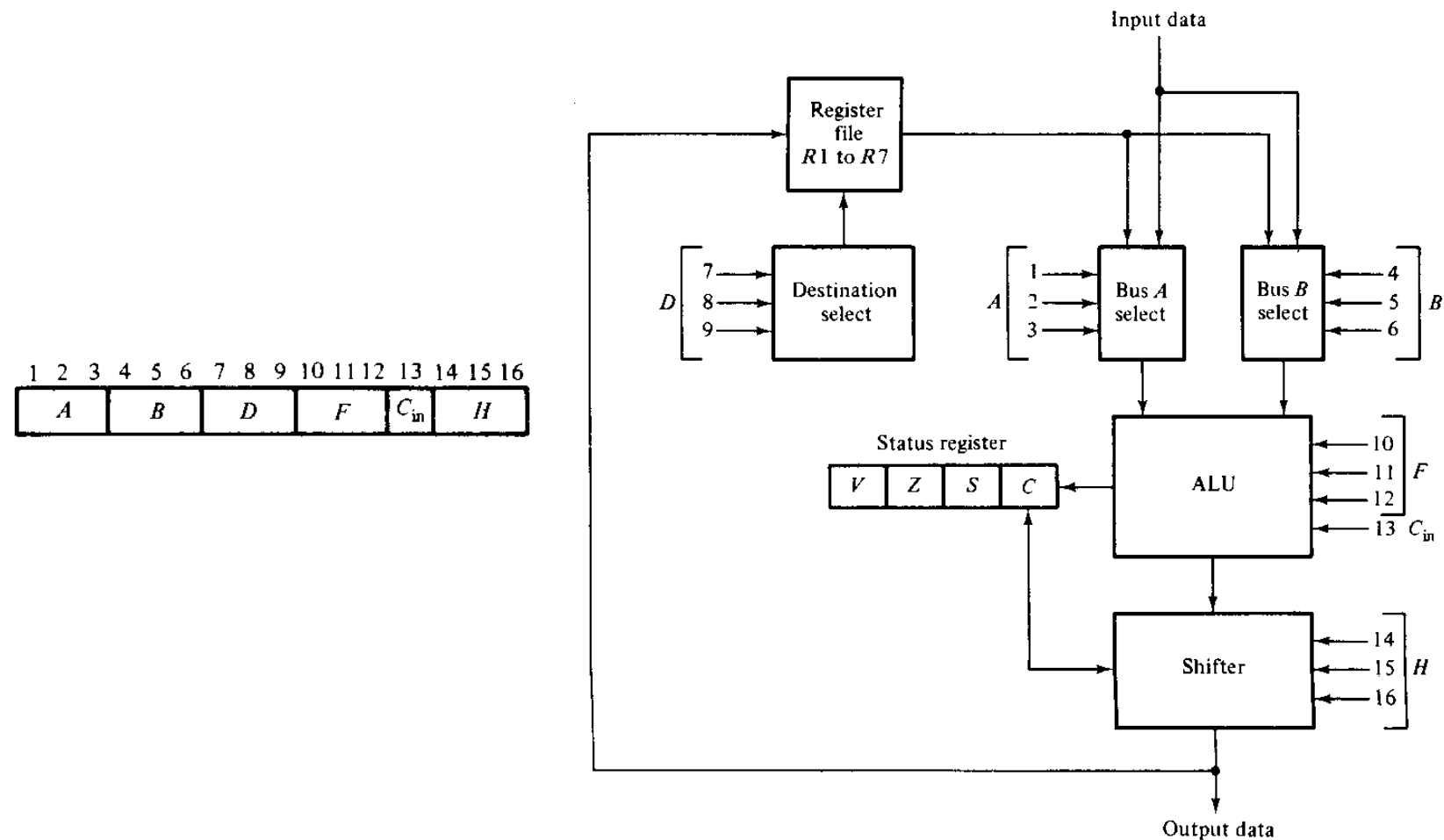

# Processor Unit

## Block Diagram with functions

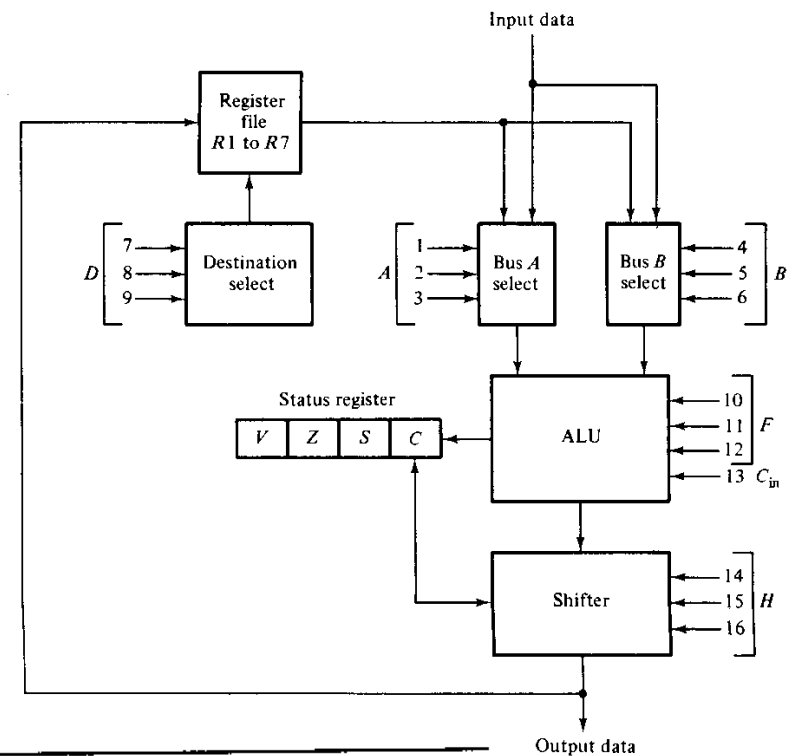

Binary code	Function of selection variables					
	<i>A</i>	<i>B</i>	<i>D</i>	<i>F</i> with $C_{in} = 0$	<i>F</i> with $C_{in} = 1$	<i>H</i>
0 0 0	Input data	Input data	None	$A, C \leftarrow 0$	$A + 1$	No shift
0 0 1	<i>R1</i>	<i>R1</i>	<i>R1</i>	$A + B$	$A + B + 1$	Shift-right, $I_R = 0$
0 1 0	<i>R2</i>	<i>R2</i>	<i>R2</i>	$A - B - 1$	$A - B$	Shift-left, $I_L = 0$
0 1 1	<i>R3</i>	<i>R3</i>	<i>R3</i>	$A - 1$	$A, C \leftarrow 1$	0's to output bus
1 0 0	<i>R4</i>	<i>R4</i>	<i>R4</i>	$A \vee B$	—	—
1 0 1	<i>R5</i>	<i>R5</i>	<i>R5</i>	$A \oplus B$	—	Circulate-right with <i>C</i>
1 1 0	<i>R6</i>	<i>R6</i>	<i>R6</i>	$A \wedge B$	—	Circulate-left with <i>C</i>
1 1 1	<i>R7</i>	<i>R7</i>	<i>R7</i>	$\bar{A}$	—	—

# Processor Unit

## □ Examples of Micro-operations

Microoperation	Control word						Function
	<i>A</i>	<i>B</i>	<i>D</i>	<i>F</i>	<i>C<sub>in</sub></i>	<i>H</i>	
$R1 \leftarrow R1 - R2$	001	010	001	010	1	000	Subtract $R2$ from $R1$
$R3 \sim R4$	011	100	000	010	1	000	Compare $R3$ and $R4$
$R5 \leftarrow R4$	100	000	101	000	0	000	Transfer $R4$ to $R5$
$R6 \leftarrow \text{Input}$	000	000	110	000	0	000	Input data to $R6$
$\text{Output} \leftarrow R7$	111	000	000	000	0	000	Output data from $R7$
$R1 \leftarrow R1, C \leftarrow 0$	001	000	001	000	0	000	Clear carry bit $C$
$R3 \leftarrow \text{shl } R3$	011	011	011	100	0	010	Shift-left $R3$ with $I_L = 0$
$R1 \leftarrow \text{crc } R1$	001	001	001	100	0	101	Circulate-right $R1$ with carry
$R2 \leftarrow 0$	000	000	010	000	0	011	Clear $R2$

# Processor Unit

## ❑ Other operations

- How to shift the contents of a specific register?
- **How to clear a specific register?**
  - There are several ways to perform these operations
  - We need to find the simplest one.


# Lesson-16:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Design of Accumulator	<ul style="list-style-type: none"><li>• To identify the requirements of accumulator design</li><li>• To design an accumulator using JK flipflop.</li></ul>	Class Lecture Question and answer	Test, exams, quiz, etc

# Design of Accumulator
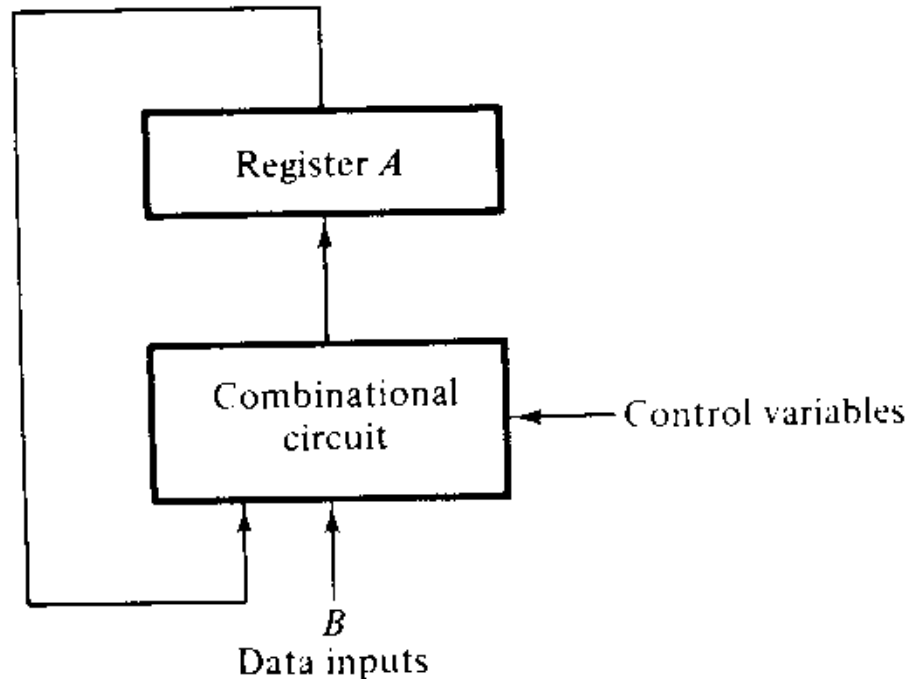
## □ Accumulator

- Not only the 'register A' but the combinational circuit is also a part of the accumulator.



# Design of Accumulator

## □ Accumulator

- A multi-functional register
  - **Not only perform the operations of commonly used register.**
  - **It should be perform all the micro-operations in a processor unit.**
  - **Also termed as multipurpose operational register.**
  - **The design of accumulator is dependent on the number of micro-operations it should be performed.**

# Design of Accumulator

## □ List of micro operations for an accumulator

Control variable	Microoperation	Name
$p_1$	$A \leftarrow A + B$	Add
$p_2$	$A \leftarrow 0$	Clear
$p_3$	$A \leftarrow \bar{A}$	Complement
$p_4$	$A \leftarrow A \wedge B$	AND
$p_5$	$A \leftarrow A \vee B$	OR
$p_6$	$A \leftarrow A \oplus B$	Exclusive-OR
$p_7$	$A \leftarrow \text{shr } A$	Shift-right
$p_8$	$A \leftarrow \text{shl } A$	Shift-left
$p_9$	$A \leftarrow A + 1$	Increment
	If ( $A = 0$ ) then ( $Z = 1$ )	Check for zero



# Design of Accumulator

## □ Design procedure

- Each stage of the accumulator should be designed separately
  - **Stages  $A_i$  should be connected in sequence  $i=1, \dots, n$ .**
  - **Each stage should be designed with a flip-flop**
    - **In this example we will use JK flip-flop,**
    - **Characteristics of JK flip-flop**

$$Q(t+1) = JQ' + K'Q$$


- **Control variables should be mutually exclusive.**

# Design of Accumulator


## □ Design procedure

- Add **B** to **A**
  - Control variable  $p_1$

Present state	Inputs		Next state	Flip-flop inputs		Output
$A_i$	$B_i$	$C_i$	$A_i$	$JA_i$	$KA_i$	$C_{i+1}$
0	0	0	0	0	X	0
0	0	1	1	1	X	0
0	1	0	1	1	X	0
0	1	1	0	0	X	1
1	0	0	1	X	0	0
1	0	1	0	X	1	1
1	1	0	0	X	1	1
1	1	1	1	X	0	1

 

$$JA_i = B_i C_i' + B_i' C_i$$

 

$$KA_i = B_i C_i' + B_i' C_i$$



$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

# Design of Accumulator

## □ Design procedure

- Add **B** to **A** (control variable  $p_1$ )
  - The Boolean function with control variable

$$JA_i = B_i C_i' p_1 + B_i' C_i p_1$$

$$KA_i = B_i C_i' p_1 + B_i' C_i p_1$$

$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

# Design of Accumulator

## □ Design procedure

### – Clear **A** ( $p_2$ )

- We need only apply control variable to K.

$$Q(t+1) = JQ' + K'Q$$

- The Boolean function

$$JA_i = 0$$

$$KA_i = p_2$$

### – Complement ( $p_3$ )

- The Boolean function

$$JA_i = p_3$$


$$KA_i = p_3$$

# Design of Accumulator

## □ Design procedure


– AND ( $p_4$ )

Present state	Input	Next state	Flip-flop inputs	
$A_i$	$B_i$	$A_i$	$JA_i$	$KA_i$
0	0	0	0	X
0	1	0	0	X
1	0	0	X	1
1	1	1	X	0

 

– OR ( $p_5$ )

Present state	Input	Next state	Flip-flop inputs	
$A_i$	$B_i$	$A_i$	$JA_i$	$KA_i$
0	0	0	0	X
0	1	1	1	X
1	0	1	X	0
1	1	1	X	0

 


# Design of Accumulator

## □ Design procedure

– XOR ( $p_6$ )

Present state	Input	Next state	Flip-flop inputs	
$A_i$	$B_i$	$A_i$	$JA_i$	$KA_i$
0	0	0	0	X
0	1	1	1	X
1	0	1	X	0
1	1	0	X	1

 

– Shift right ( $p_7$ )

$$JA_i = A_{i+1}p_7$$

$$KA_i = A'_{i+1}p_7$$

– Shift left ( $p_8$ )


$$JA_i = A_{i-1}p_8$$

$$KA_i = A'_{i-1}p_8$$

# Design of Accumulator
 
## □ Design procedure

- Increment ( $p_9$ )
  - Similar with synchronous counter of fig. 7-17




$$\begin{aligned}
 JA_i &= E_i \\
 KA_i &= E_i \\
 E_{i+1} &= E_i A_i \quad i = 1, 2, \dots, n \\
 E_1 &= p_9
 \end{aligned}$$

# Design of Accumulator

## □ Design procedure

- Check for zero (**Z**)

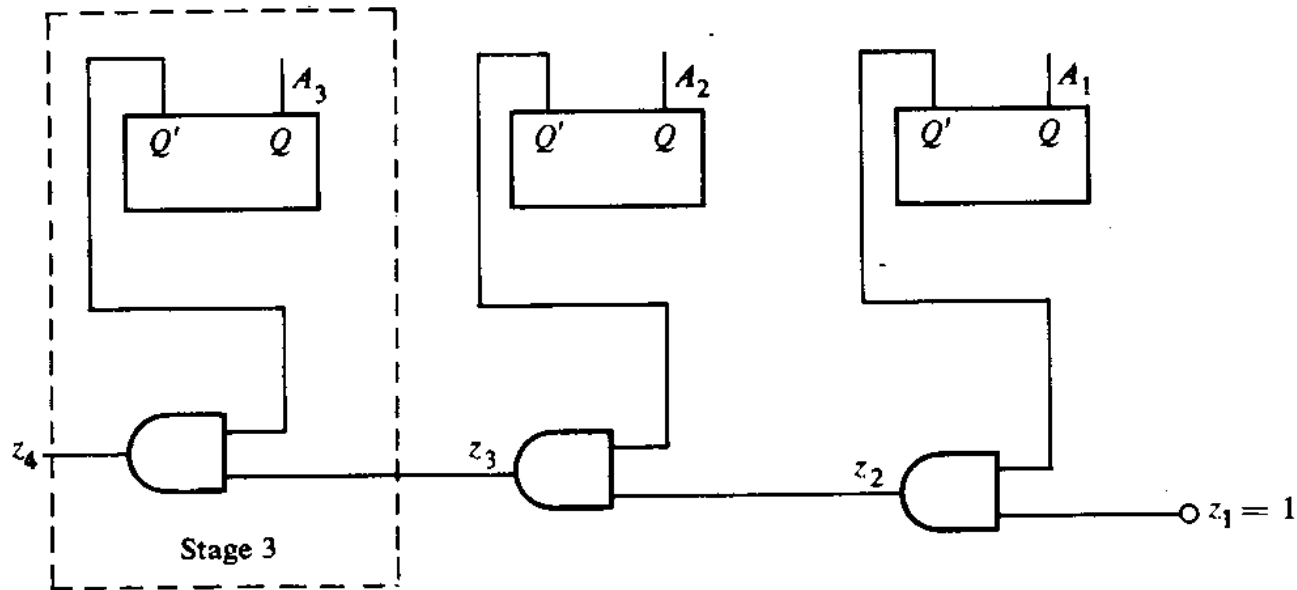

$$z_{i+1} = z_i A'_i \quad i = 1, 2, \dots, n$$

$$z_1 = 1$$

$$z_{n+1} = Z$$



# Design of Accumulator

## □ Design procedure

- One stage of accumulator

$$JA_i = B_i C'_i p_1 + B'_i C_i p_1 + p_3 + B_i p_5 + B_i p_6 + A_{i+1} p_7 + A_{i-1} p_8 + E_i$$

$$KA_i = B_i C'_i p_1 + B'_i C_i p_1 + p_2 + p_3 + B'_i p_4 + B_i p_6 + A'_{i+1} p_7 \\ + A'_{i-1} p_8 + E_i$$


$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

$$E_{i+1} = E_i A_i$$

$$z_{i+1} = z_i A'_i$$
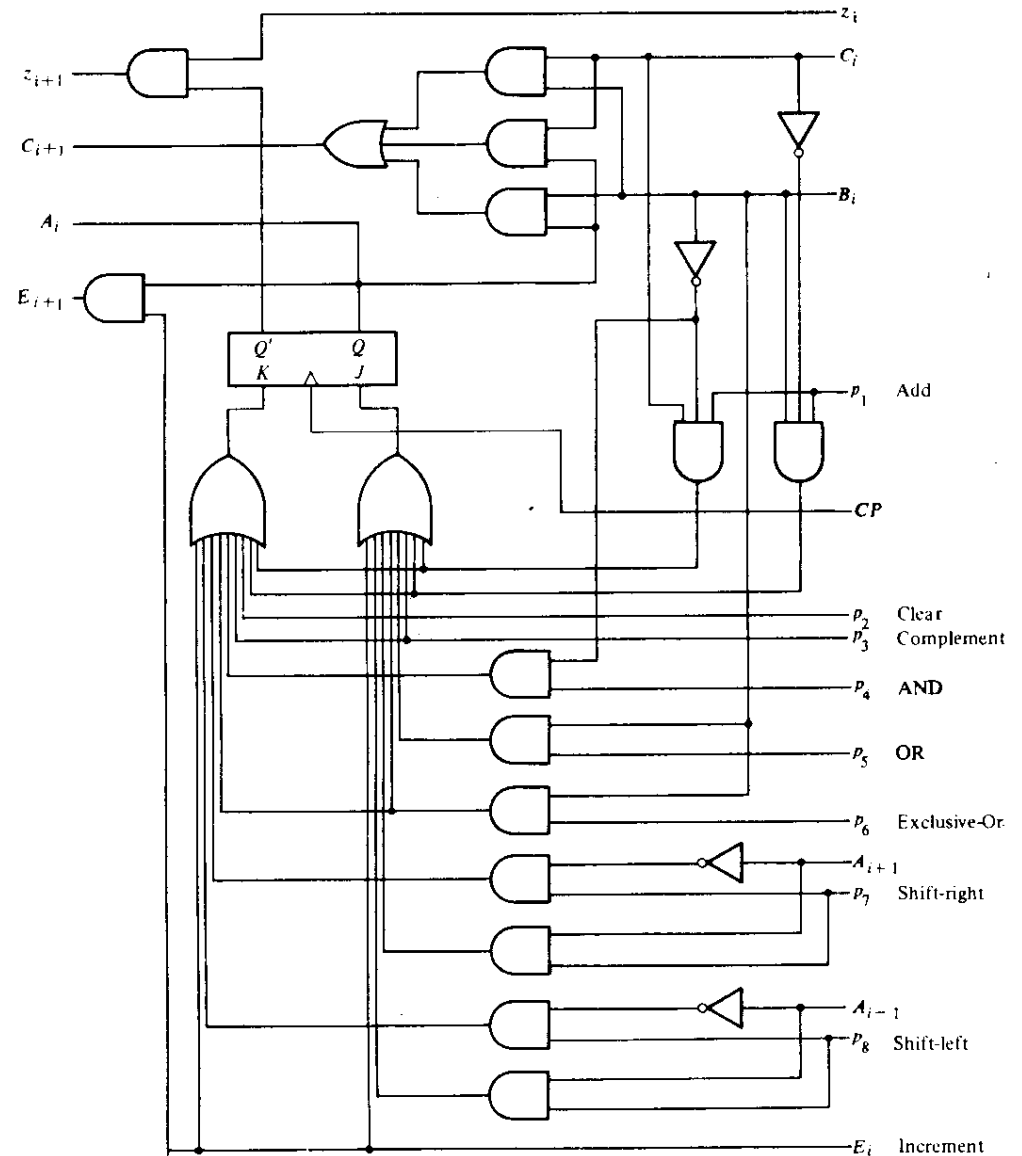
# Design of Accumulator


- Design procedure
  - One stage of accumulator



# Design of Accumulator
 
## □ Design procedure

- Complete accumulator
- 4-bit accumulator with 4 stages



# Lesson-17:

Topic	Lesson Learning Outcomes	Teaching-Learning Methodology	Assessment Method
Solving problems of Chapter-9	<ul style="list-style-type: none"><li>To improve the problem solving skills</li></ul>	Class Lecture Homework	Test, exams, quiz, assignment, etc